



An MoE Govt of India Initiative




Non Inverting Opamp

INSTRUCTION

EXPERIMENTAL TABLE

Resistance: 10 K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	-90.0	-0.100
2	-10	-60.0	-0.0667
3	-5	-30.0	-0.0333
4	0	0.00	0.00
5	5	30.0	0.0333

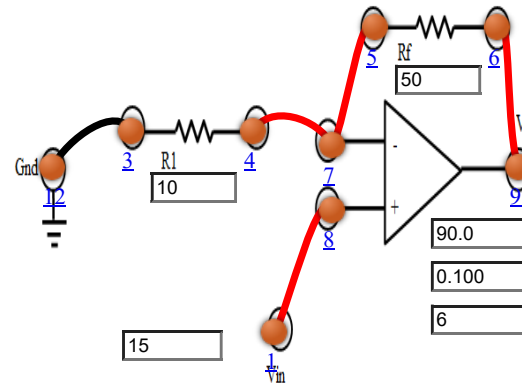

CONTROLS

Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f): Kohms

Add to Table


Plot

Clear

Check
connectionDelete all
connection

GRAPH PLOT

Vo-Vi Plot

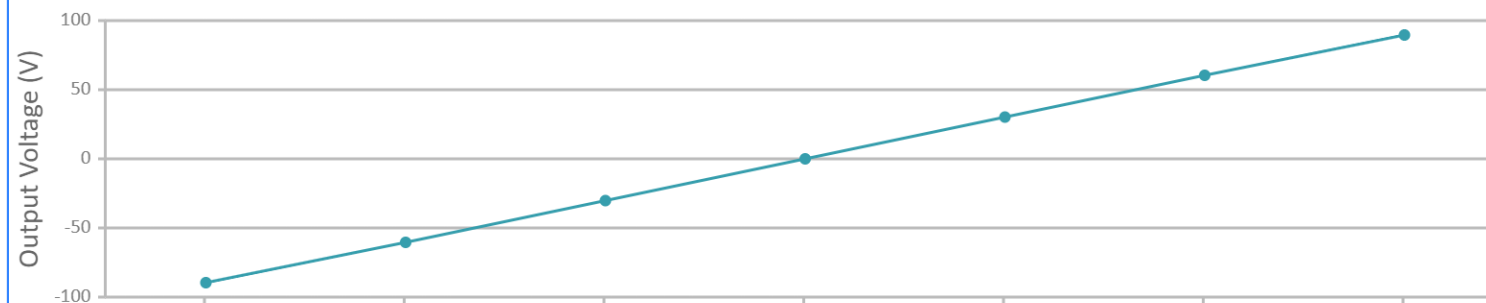

Print

